

Biophysical Background



Biophysics Background

Bioengineering 6460 Bioelectricity

The Basics

- **Materials**
 - Conductor, capacitors
- **Ohm's Law and Circuits**
 - Ohms law, IV curves, dynamic circuit analysis
- **Fields**
 - Electric field, potential field
- **Sources, Sinks, and Vector Calculus**
 - Current monopoles, dipoles
 - Volume conductor fields
 - Div, grad, curl and all that




Biophysics Background

Bioengineering 6460 Bioelectricity

Conductors & Resistors

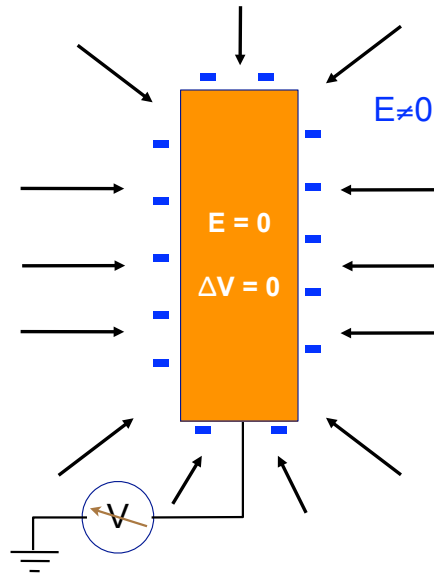- **Conductors**
 - Electrons free to move
 - Current flow in response to electric field
 - In static state, no net charge ($E=0$)
- **Resistors**
 - Electrons less free to move
 - Create potential differences
 - Depend on material properties



$$R = \frac{\rho l}{A}$$



Biophysics Background

Bioengineering 6460 Bioelectricity

Capacitance



$$C = \frac{Q}{V} \quad \frac{dV}{dt} = \frac{I_c}{C}$$

- **Dielectric**
 - Charges not free to move, just shift
 - $E \neq 0$ inside, opposes applied E
 - Result is reduce v and increased C

Does anything change when the plates move?

$$Q = CV$$

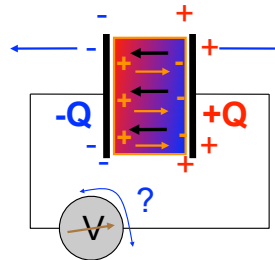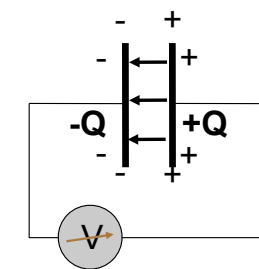
Yes, V increases while Q and E are the same so C decreases.



Biophysics Background

Bioengineering 6460 Bioelectricity


Membrane Equivalent Circuit

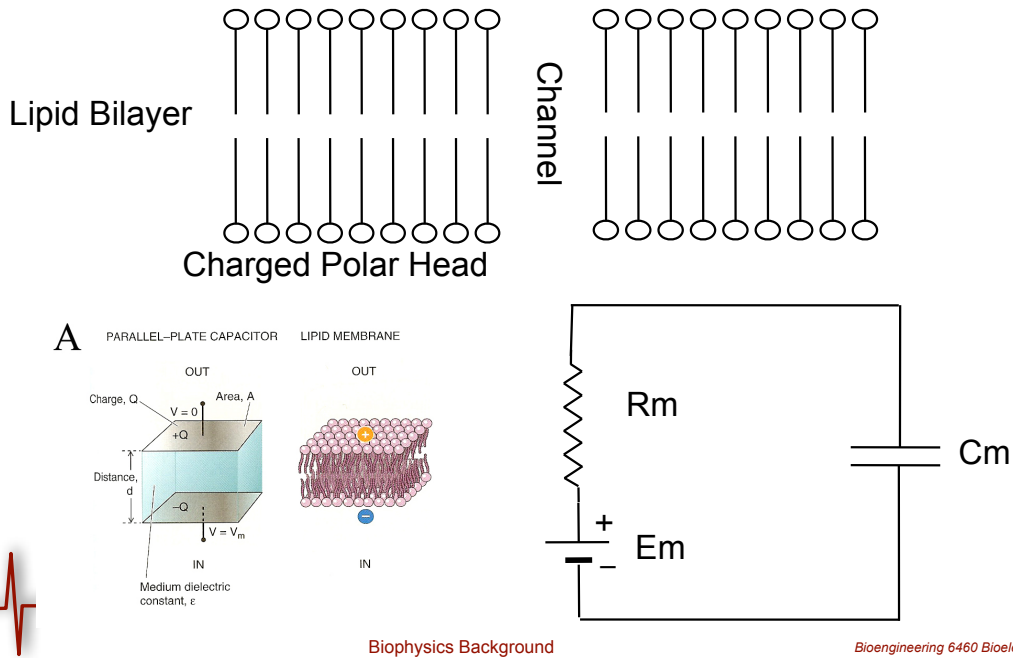



Current and Ohm's Law

- Without potential difference there is no current!
- Without conductance, there is no current.
- Ohm's law:
 - linear relationship between current and voltage
 - not universal, especially not in living systems

$$I = \frac{1}{R} V = GV$$

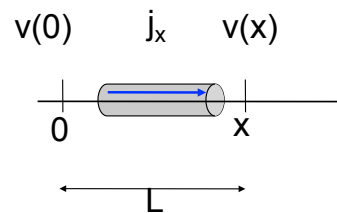


Current-Voltage (I-V) Curves

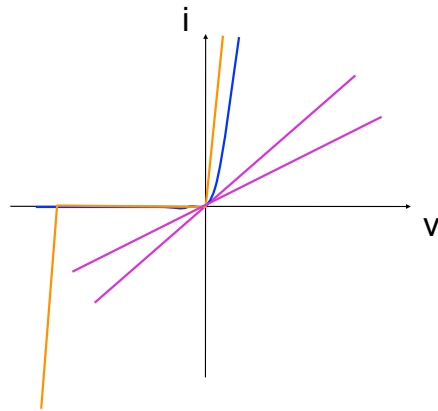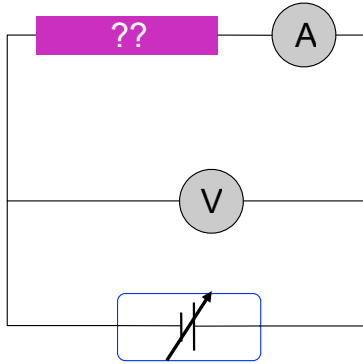

Biophysics Background

Bioengineering 6460 Bioelectricity


Equivalent circuits 1

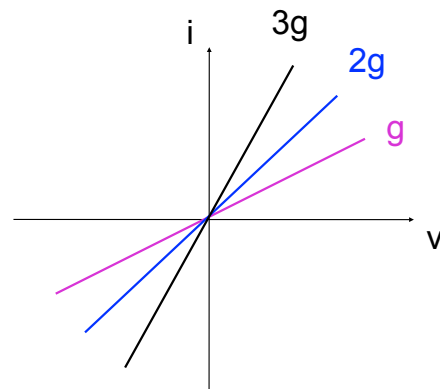

Biophysics Background

Bioengineering 6460 Bioelectricity


Equivalent circuits 2

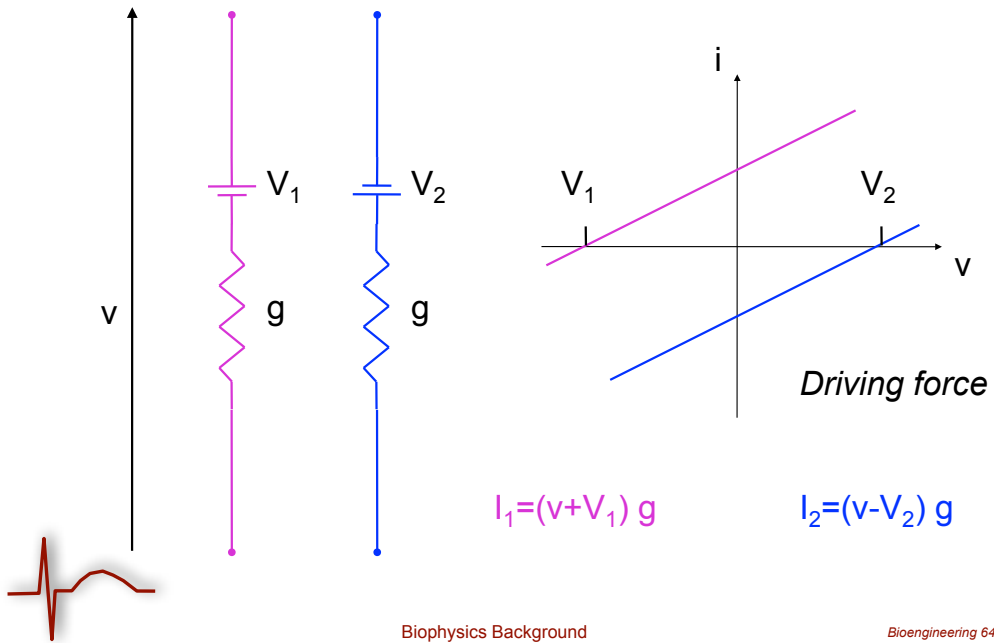

Biophysics Background

Bioengineering 6460 Bioelectricity

I-V Curve Examples


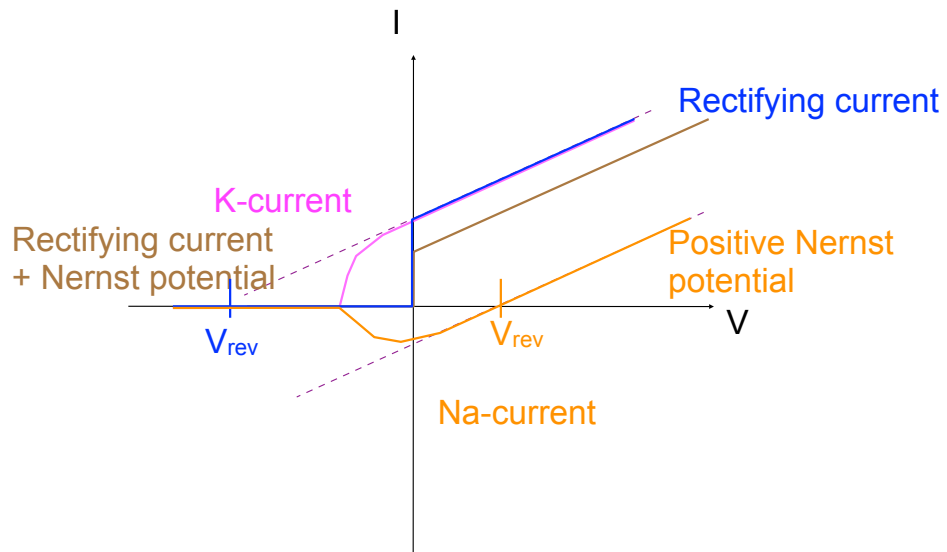


Biophysics Background

Bioengineering 6460 Bioelectricity

Circuit Analysis

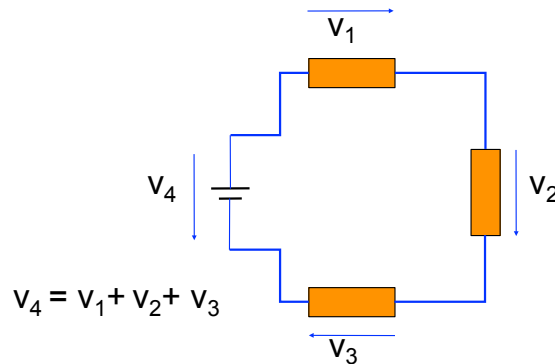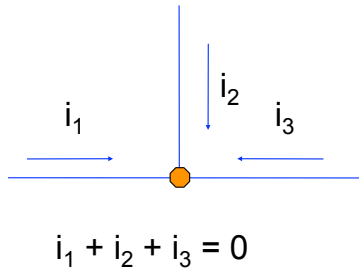- Conservation of charge: currents sum at nodes
- Conservation of energy: sum of voltages = 0




Voltage Divider

$$i = V_B / (R_1 + R_2)$$

$$i = V_2 / R_2$$

$$V_2 = V_B R_2 / (R_1 + R_2)$$

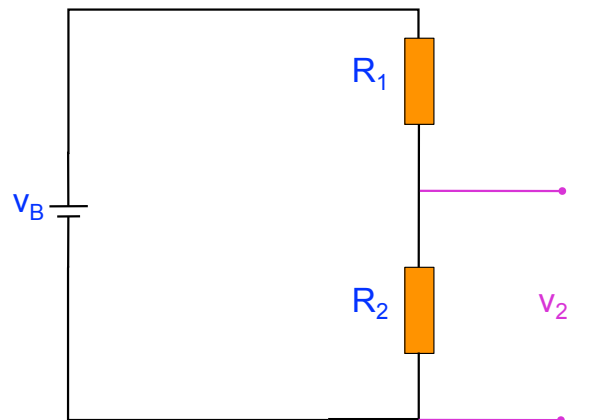

Examples of voltage dividers in EP measurements?

Electrical Profile of a Cell

